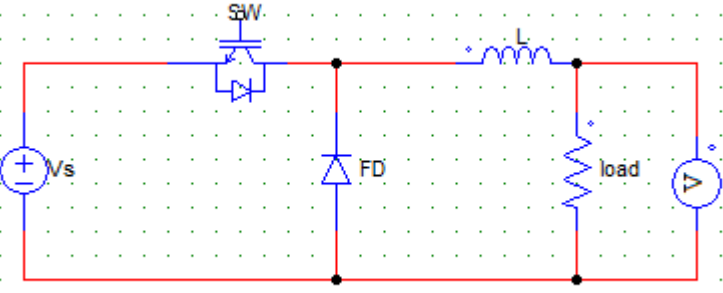
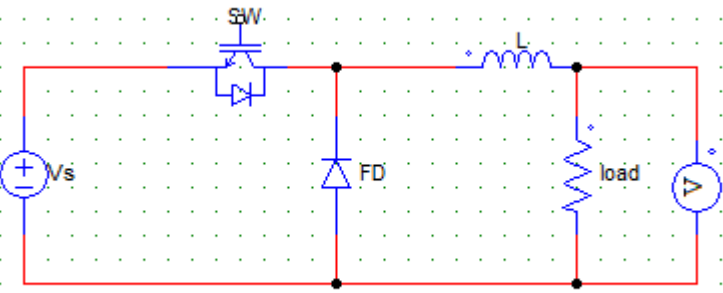
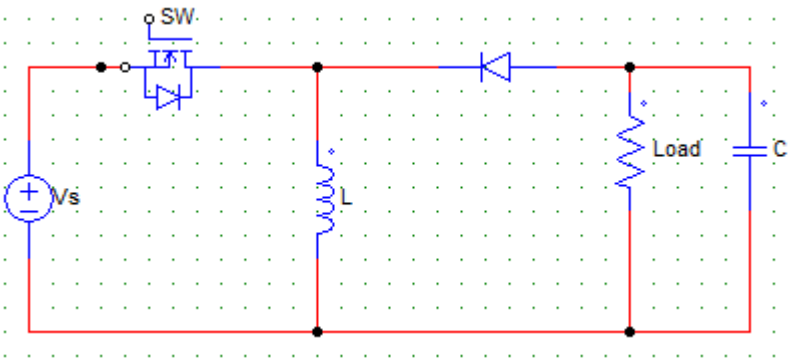
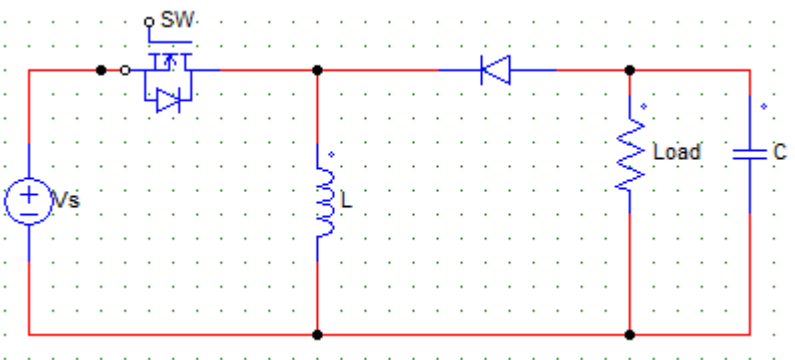
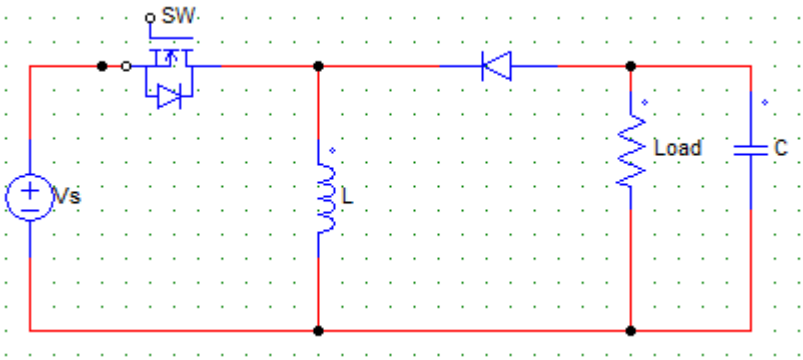
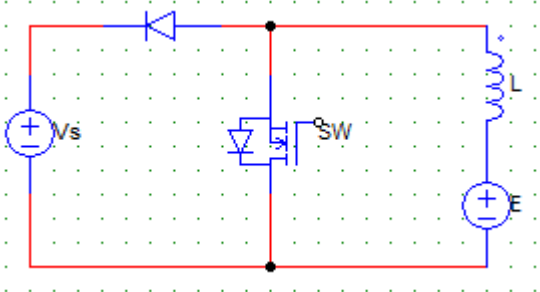
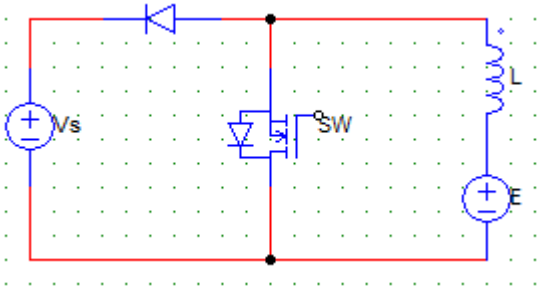
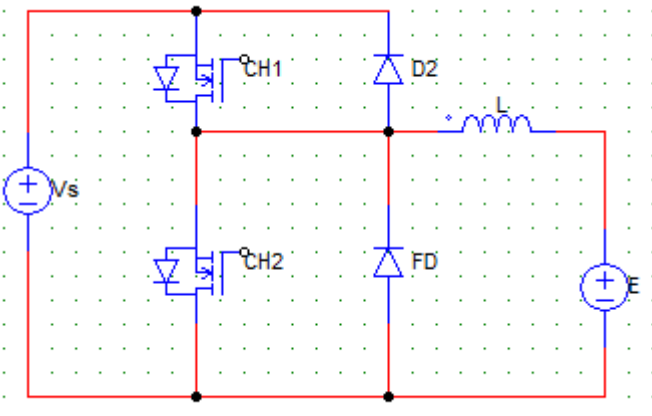
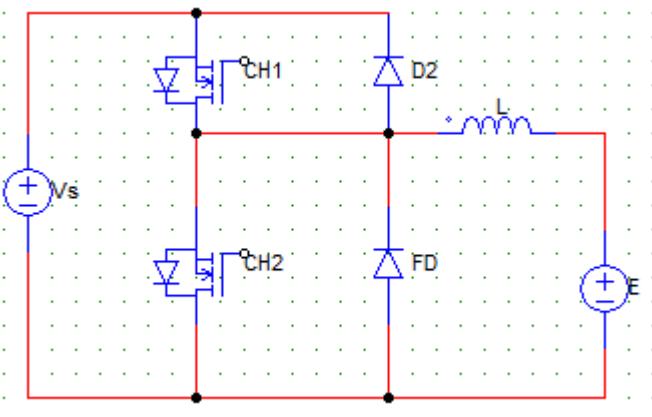


	Power Electronics (EE 5th Semester) Unit 3: CHOPPERS
1	Choppers converter a) AC to DC b) DC to AC c) DC to DC d) AC to AC
2	A chopper may be thought as a a) Inverter with DC input b) DC equivalent of an AC transformer c) Diode rectifier d) DC equivalent of an induction motor
3	Which device can be used in a chopper circuit? a) BJT b) MOSFET c) GTO d) All of the mentioned
4	A chopper is a a) Time ratio controller b) AC to DC converter c) DC transformer d) High speed semiconductor switch
5	What is the duty cycle of a chopper? a) T_{on}/T_{off} b) T_{on}/T c) T/T_{on} d) $T_{off} \times T_{on}$
6	The load voltage of a chopper can be controlled by varying the a) duty cycle b) firing angle c) reactor position d) extinction angle
7	The values of duty cycle (α) lies between a) $0 < \alpha < 1$ b) $0 > \alpha > -1$ c) $0 \leq \alpha \leq 1$ d) $1 < \alpha < 100$
8	If T is the time period for a chopper circuit and α is its duty cycle, then the chopping frequency is a) T_{on}/α b) T_{off}/α c) α/T_{off} d) α/T_{on}
9	Find the output voltage expression for a step down chopper with V_s as the input voltage and α as the duty cycle. a) $V_o = V_s/\alpha$ b) $V_o = V_s \times \alpha$

	c) $V_o = V_s^2/\alpha$ d) $V_o = 2V_s/\alpha\pi$
10	The below given figure is that of a _____ (IGBT is used as a chopper switch)  a) step-up/step-down chopper b) step-down chopper c) step-up chopper d) none of the mentioned
11	If a step up chopper's switch is always kept off then (ideally) a) $V_o = 0$ b) $V_o = \infty$ c) $V_o = V_s$ d) $V_o > V_s$
12	If a step up chopper's switch is always kept open then (ideally) a) $V_o = 0$ b) $V_o = \infty$ c) $V_o = V_s$ d) $V_o > V_s$
13	Find the average value of output voltage of a basic step-down chopper, with duty cycle = α and load = $R \Omega$.  a) $I = V_s \times \alpha$ b) $I = (V_s \times \alpha)/R$ c) $I = 0$ d) $I = V_s/R$
14	For a step-up chopper, when the duty cycle is increased the average value of the output voltage a) increases b) decreases c) remains the same d) none of the mentioned


15	For a step-down chopper, when the duty cycle is increased the average value of the output voltage a) increases b) decreases c) remains the same d) none of the mentioned
16	The below given chopper circuit is that of a  a) step-up chopper b) step-down chopper c) step-up/step-down chopper d) none of the mentioned
17	The expression for a step-up/step-down chopper with α as the duty cycle and V_s as the dc input voltage is a) $V_s / (1 - \alpha)$ b) $\alpha \times V_s$ c) $V_s (\alpha / (1 - \alpha))$ d) $V_s (\alpha / (1 + \alpha))$
18	For a step-up/step-down chopper, if α (duty cycle) = 0.5 then a) $V_o = V_s$ b) $V_o < V_s$ c) $V_o > V_s$ d) none of the mentioned
19	In the figure shown below, the capacitor C is used to  a) maintain the load voltage constant b) protect the load c) protect the chopper switch (SW) d) maintain the load current constant
20	For a step-up/step-down chopper, if α (duty cycle) < 0.5 then a) $V_o = V_s$

	b) $V_o < V_s$ c) $V_o > V_s$ d) none of the mentioned
21	In the below shown step-up/step-down chopper circuit, when the chopper switch (SW) if first on and then off, then the current flows from path  a) V_s-CH-L-V_s b) L-Load-D-L c) L-D-Load-L d) no current flows
22	A step-down chopper is also called as a a) first-quadrant chopper b) second-quadrant chopper c) third-quadrant chopper d) fourth-quadrant chopper
23	For the type-B chopper shown below  a) during T_{on}, $V_o = 0$ and L stores energy b) during T_{on}, V_o is not 0 and L stores energy c) during T_{on}, $V_o = 0$ and L releases energy d) during T_{on}, V_o is not 0 and L releases energy
24	The below given chopper is that of a  a) step-up chopper b) step-down chopper

	c) step-up/step-down chopper d) depends on the duty cycle
25	The type-C chopper or two quadrant type-A chopper has a) type-A and type-B choppers in series b) type-A and type-B choppers in parallel c) two type-A choppers in series d) two type-A choppers in parallel
26	In case of TRC (Time Ratio Control), _____ is varied a) duty cycle b) firing angle c) supply frequency d) supply voltage magnitude
27	Name the below given circuit.  a) Type D chopper b) Type B chopper c) Two-quadrant type A chopper d) Two-quadrant type B chopper
28	In the below given circuit output voltage will be 0 when  a) SW1 is on b) FD is not conducting c) D2 is conducting d) SW2 is on

29


In the below given circuit

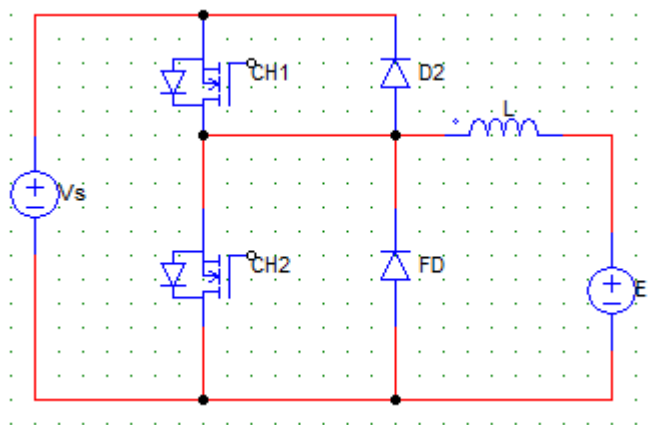

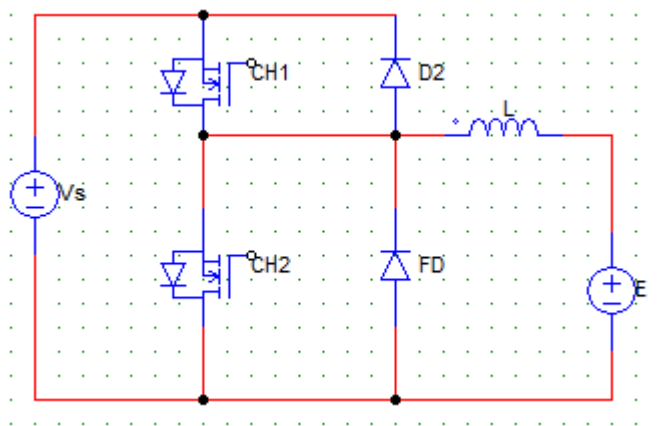- a) current can never be zero
- b) **current can flow in both the directions of the load**
- c) voltage can never be zero
- d) none of the mentioned

30


In the below given type C chopper circuit, _____ and _____ together operate like type A chopper.




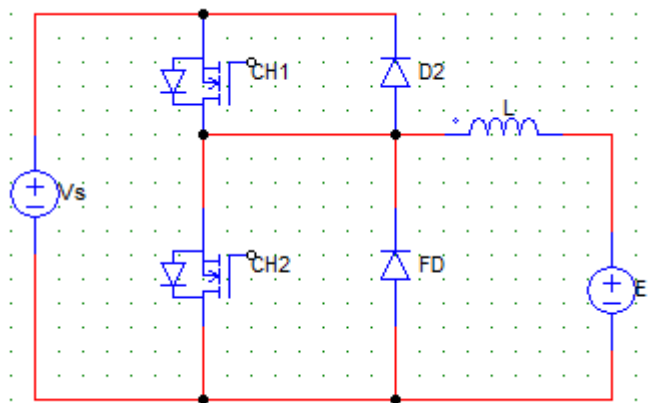
- a) **CH1, FD**
- b) CH2, FD
- c) CH1, D2
- d) CH2, D2


31



In the below given type C chopper circuit, _____ and _____ together operate like type B chopper.





	a) CH1, FD b) CH2, FD c) CH1, D2 d) CH2, D2
32	Which type of chopper is used in the regenerative braking of DC motors? a) type A b) type B c) type C d) type D
33	Type C chopper consists of a) two diodes and two switches b) one diode and one switch c) one diode and three switches d) three diodes and two switches
34	In a type C chopper, if only one switch is operated a) only one quadrant operation will be obtained b) two quadrant operation can be obtained c) the chopper won't work d) none of the mentioned
35	A type D chopper is a a) two quadrant type-B chopper b) two quadrant type-A chopper c) two quadrant type-C chopper d) none of the mentioned
36	In a type-D chopper a) current can flow in both the directions of the load b) current cannot flow in both the directions of the load c) voltage can only be positive d) voltage can only be negative
37	For a type D chopper, the average value of output voltage will be positive when a) $T_{on} = T_{off}$ b) $T_{on} < T_{off}$ c) $T_{off} = 0$ d) $T_{on} > T_{off}$
38	For a type D chopper, if duty cycle = 0.5 then the a) average voltage is positive b) average voltage is negative c) average voltage is zero d) chopper cannot be operated with duty cycle = 0.5

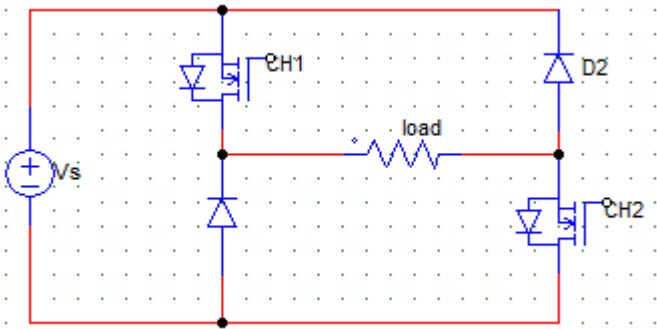
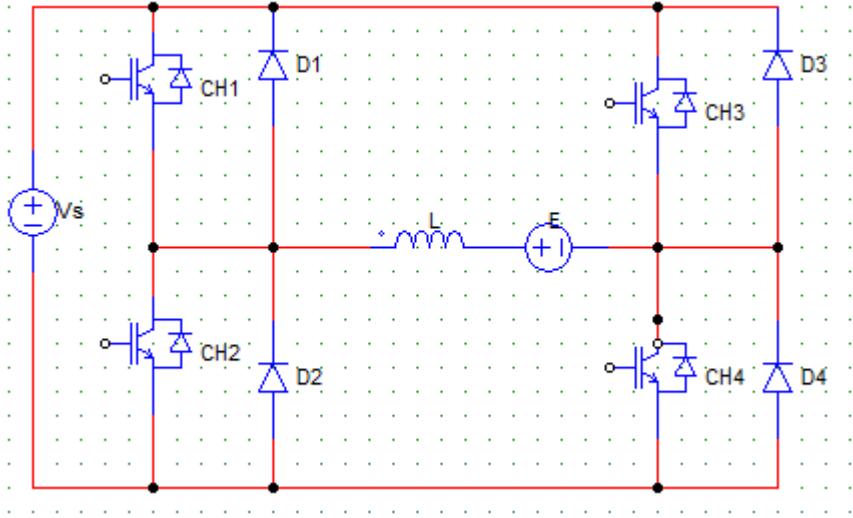
39	In the below given circuit, if only SW1 is operated then  a) the power flows from load to source b) the power flows from source to load c) the average voltage is positive d) none of the mentioned
40	For a type D chopper, if duty cycle $\alpha < 0.5$ then the a) average voltage is positive b) average voltage is negative c) average voltage is zero d) none of the mentioned
41	Identify the given circuit  a) type D chopper b) two quadrant type C chopper c) type E chopper d) type F chopper
42	A type C chopper consists of _____ diodes and _____ switches in anti-parallel. a) 2, 2 b) 3, 3 c) 4, 4 d) 3, 4
43	A type C chopper can operate in a) Ist and IInd quadrants b) IInd and IIIrd quadrants

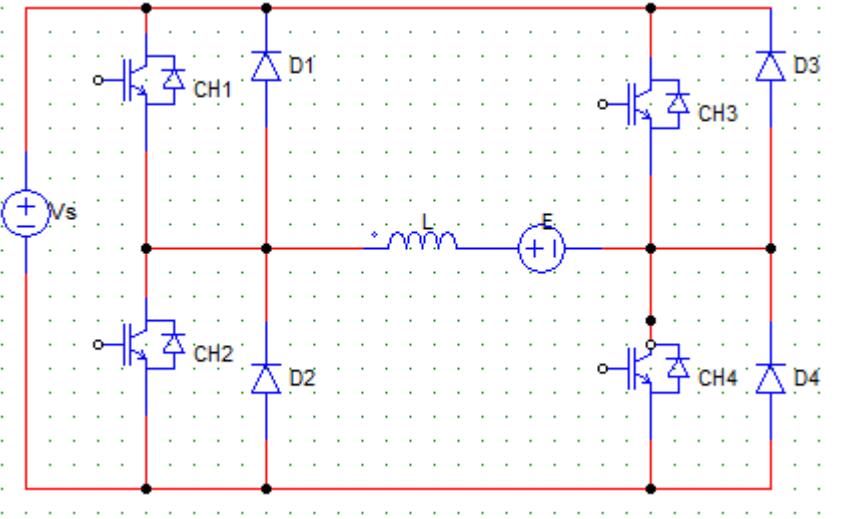
	c) Ist, IIInd and IIIrd quadrants d) all the four quadrants
44	For the first quadrant operation of type E chopper  a) Only CH1 is on b) CH1 and CH2 is on c) CH1 and CH3 is on d) CH1 and CH4 is on
45	What is the expression for load voltage when the chopper is operated in the second quadrant? a) V_s b) E c) 0 d) $E + L \frac{di}{dt}$
46	The load emf E must be reversed for a) first and second quadrant operation b) third quadrant operation c) fourth quadrant operation d) both third and fourth quadrant operation
47	For the type E chopper to be operated in the fourth quadrant a) only one switch is operated b) two switches are operated c) three switches are operated d) all the switches are operated
48	In a type E chopper, if all the four chopper switches are closed simultaneously then a) load is short circuited b) supply is short circuited c) both load and supply are shorted d) none of the mentioned.

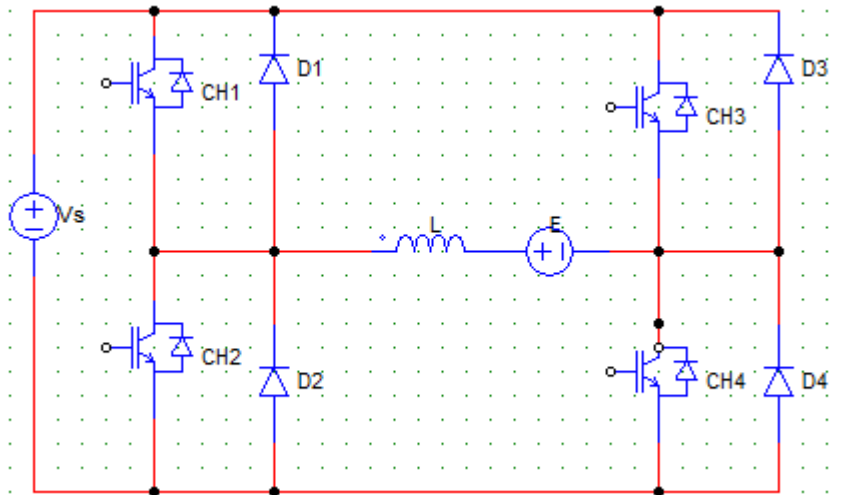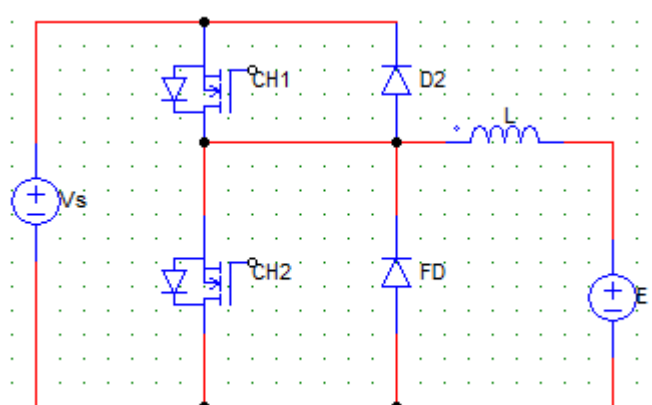49	When CH4 is turned on and then off  a) load current falls to zero b) negative current freewheels through D2, D3 c) positive current freewheels through D2, D3 d) none of the mentioned
50	A type C chopper is operated with only positive load current. Choose the correct statement.  a) CH1 would remain idle b) D2 would remain idle c) CH2 would remain idle d) Both D2 and CH2 would remain idle

Unit 4: INVERTERS AND UPS	
1	Inverters converts a) dc power to dc power b) dc power to ac power c) ac power to ac power d) ac power to dc power
2	Line-commutated inverters have a) AC on the supply side and DC on the load side b) AC on both supply and load side

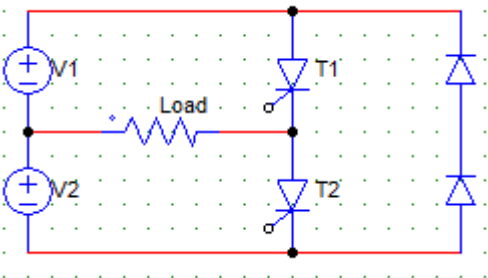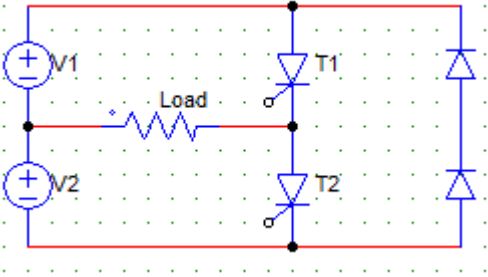	c) DC on both supply and load side d) DC on the supply side and AC on the load side
3	In a VSI (Voltage source inverter) a) the internal impedance of the DC source is negligible b) the internal impedance of the DC source is very very high c) the internal impedance of the AC source is negligible d) the IGBTs are fired at 0 degrees.
4	_____ based inverters do not require self-commutation. a) IGBT b) GTO c) PMOSFET d) SCR
5	Identify the circuit given below.  a) Half wave series inverter b) Full wave series inverter c) Half wave bridge inverter d) Half wave parallel inverter
6	Single phase half bridge inverters requires a) two wire ac supply b) two wire dc supply c) three wire ac supply d) three wire dc supply
7	What is the voltage across the R load when only T1 is conducting?  a) V_s b) $V_s/2$ c) $2V_s$ d) zero
8	In a single-phase half wave inverter _____ SCR(s) are/is gated at a time. a) one b) two c) three d) none of the mentioned

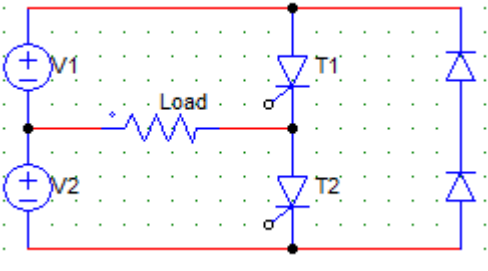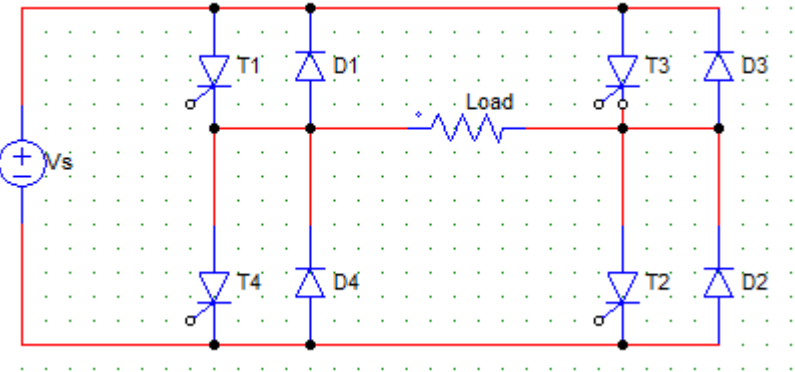9	What is the voltage across the R load when only T2 is conducting?  a) V_s b) $V_s/2$ c) $2V_s$ d) Zero
10	The voltage in a single phase half wave inverter varies between a) V_s and 0 b) $V_s/2$ and 0 c) $V_s/2$ and $-V_s/2$ d) V_s and $-V_s$
11	The output of a single-phase half bridge inverter on R load is ideally a) a sine wave b) a square wave c) a triangular wave d) constant dc
12	The output current wave of a single-phase full bridge inverter on RL load is a) a sine wave b) a square wave c) a triangular wave d) constant dc
13	Single-phase full bridge inverters requires a) 4 SCRs and 2 diodes b) 4 SCRs and 4 diodes c) 2 SCRs and 4 diodes d) 2 SCRs and 2 diodes
14	Identify the circuit given below.  a) Full wave series inverter b) Half wave series inverter c) Full wave bridge inverter d) Full wave parallel inverter

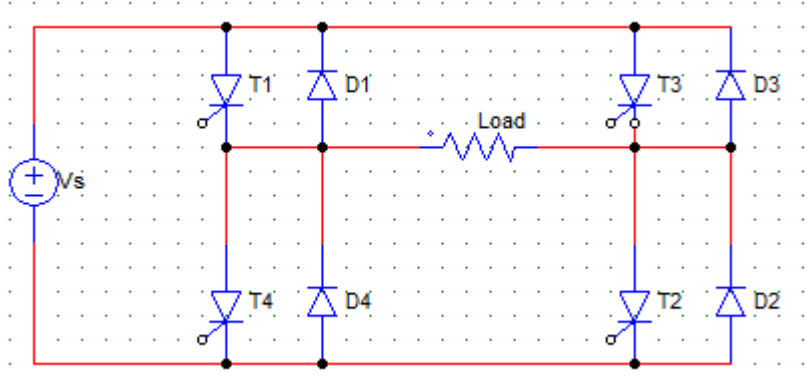
15	The output voltage from a single phase full wave bridge inverter varies from a) V_s to $-V_s$ b) V_s to zero c) $V_s/2$ to zero d) $-V_s/2$ to $V_s/2$
16	In a single phase full wave bridge inverter, when the output is V_s or $-V_s$ a) one SCR and one diode are conducting b) four SCRs are conducting c) two SCRs are conducting d) two diodes are conducting
17	In the following circuit, the diodes D1 to D4 are used to  a) reduce the switching losses b) send current back to the dc source when SCRs are off c) send current back to the load when SCRs are off d) send current back to the dc source when SCRs are conducting
18	For a full wave bridge inverter, the output voltage (V_o) a) $V_o = V_s/2$ for $0 < t < T/2$ b) $V_o = V_s$ for $0 < t < T/2$ c) $V_o = V_s$ for $T/2 < t < T$ d) $V_o = -V_s$ for $T/2 < t < 3T/2$
19	For a half wave bridge inverter, the output voltage a) $V_o = -V_s/2$ for $0 < t < T/2$ b) $V_o = -V_s/2$ for $T/2 < t < T$ c) $V_o = -V_s$ for $0 < t < T/2$ d) $V_o = V_s/2$ for $T/2 < t < T$
20	In a half wave circuit, forced commutation is essential when the a) load is inductive b) load is resistive c) source voltage is below 150 V d) none of the mentioned
21	In VSI (voltage source inverters) a) both voltage and current depend on the load impedance b) only voltage depends on the load impedance c) only current depends on the load impedance d) none of the mentioned
22	In the single-pulse width modulation method, the output voltage waveform is symmetrical about _____ a) π



	b) 2π c) $\pi/2$ d) $\pi/4$
23	In the single-pulse width modulation method, the output voltage waveform is symmetrical about _____ in the negative half cycle. a) 2π b) $3\pi/2$ c) $\pi/2$ d) $3\pi/4$
24	The shape of the output voltage waveform in a single PWM is a) square wave b) triangular wave c) quasi-square wave d) sine wave
25	A three-phase bridge inverter requires minimum of _____ switching devices. a) 3 b) 4 c) 6 d) 8
26	In the three-phase bridge inverter, each step consists of a) 30° b) 60° c) 90° d) will depend on the value of the firing angle
27	In inverters, to make the supply voltage constant a) an inductor is placed in series with the load b) capacitor is connected in parallel to the load side c) capacitor is connected in parallel to the supply side d) none of the mentioned
28	In the 180° mode VSI, _____ devices conduct at a time. a) 5 b) 2 c) 3 d) 4
29	In voltage fed thyristor inverters _____ commutation is required. a) load b) forced c) self d) any commutation technique can be used
30	What is the maximum line voltage value in case of a three-phase VSI in 180° mode? a) $2V_s$ b) V_s c) $3V_s$ d) $2V_s/3$
31	The 120° mode of operation of a three phase bridge inverter requires _____ number of steps. a) 2 b) 4

	c) 6 d) 8
32	In case of the 120° mode of operation, _____ devices conduct at a time. a) 2 b) 3 c) 4 d) none of the mentioned
33	Safe commutation can be achieved in case of the _____ operating mode. a) 180° b) 120° c) 360° d) none of the mentioned
34	Several equidistant pulses per half cycle are used in _____ type of modulation technique. a) single-pulse b) multiple-pulse c) sine-pulse d) equidistant-pulse
35	In the MPM method, the comparator is given _____ and _____ types of waveform at its input. a) square, sine b) square, quasi-square c) sine, triangular d) square, triangular
36	In MPM, the square wave is the _____ signal whereas the triangular wave is the _____ signal. a) reference, carrier b) base, reference c) carrier, reference d) none of the mentioned
37	In the multiple pulse width modulation method, the firing pulses are generate during the interval when the a) triangular wave exceeds the square modulating wave b) square modulating wave exceeds the triangular wave c) square wave amplitude is same as the triangular wave's amplitude d) none of the mentioned
38	In _____ type of modulation method, the pulse width is not equal for all the pulses. a) multiple pulse width modulation b) single pulse width modulation c) sinusoidal pulse width modulation d) none of the mentioned
39	In sinusoidal pulse width modulation, _____ wave is compared with a _____ type of wave. a) square, sinusoidal b) sinusoidal, triangular c) sinusoidal, quasi-square d) none of the mentioned
40	In the sinusoidal pulse width modulation, _____ is the carrier wave signal. a) square wave

	b) triangular wave c) sinusoidal wave d) quasi-square wave
41	In the sinusoidal pulse width modulation, _____ is the reference wave signal. a) square wave b) triangular wave c) sinusoidal wave d) quasi-square wave
42	In sinusoidal pulse width modulation, the comparator output is high when the a) triangular wave has magnitude higher than the sinusoidal wave b) sinusoidal wave has magnitude higher than the triangular wave c) triangular wave has magnitude equal to the sinusoidal wave d) none of the mentioned
43	In PWM, the comparator output is further given to a _____ a) integrator b) scr devices c) trigger pulse generator d) snubber circuit
44	The modulation index (MI) is given by V_r = peak value of the reference wave. V_c = peak value of the carrier wave. a) V_r/V_c b) V_c/V_r c) $(1 + V_c/V_r)$ d) $1/(V_c V_r)$
45	By controlling the modulation index (MI), _____ can be controlled. a) gain b) output frequency c) harmonic content of the output voltage d) cosine component of the output voltage
46	In pulse width modulated inverters, the output voltage is controlled by controlling the a) input frequency b) modulating index c) amplification factor d) none of the mentioned
47	Increasing the number of pulses (N), _____ a) reduces the output voltage amplitude b) reduces the inverter efficiency c) improves the inverter efficiency d) none of the mentioned
48	A VSI will have a better performance if its a) load inductance is small and source inductance is large b) both load inductance and source inductance are small c) both load inductance and source inductance are large d) none of the mentioned
49	Control of frequency and control of voltage in 3-phase inverters is a) possible only through inverter control circuit b) possible through the control circuit of inverter and converter



	c) possible through inverter control of frequency and through converter control for voltage d) none of the mentioned
50	Output voltage of a single-phase bridge inverter, fed from a fixed dc source is varied by a) varying the switching frequency b) pulse-width modulation c) pulse amplitude modulation d) all of the mentioned


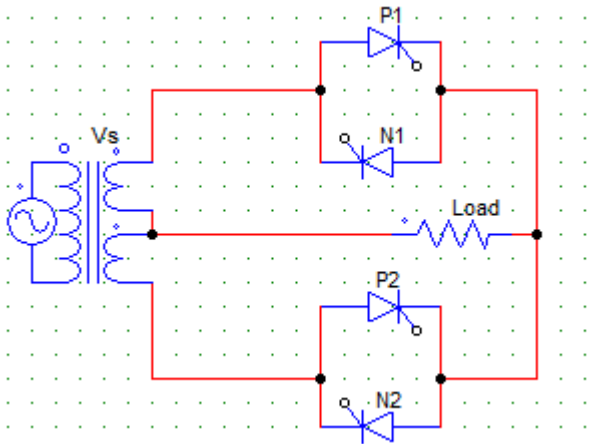
	Unit 5. CYCLOCONVERTERS
1	A cycloconverter is a _____ a) one stage power converter b) one stage voltage converter c) one stage frequency converter d) none of the mentioned
2	Applications of cycloconverters include a) speed control of ac drives b) induction heating c) static VAR compensation d) all of the mentioned
3	The single phase mid-point type cycloconverter uses _____ number of SCRs. a) 4 b) 8 c) 6 d) none of the mentioned
4	The single phase bridge type cycloconverter uses _____ number of SCRs. a) 4 b) 8 c) 6 d) none of the mentioned
5	In the positive half cycle from $\omega t = 0$ to π  a) P1 and P2 are forward biased b) N1 and P2 are forward biased

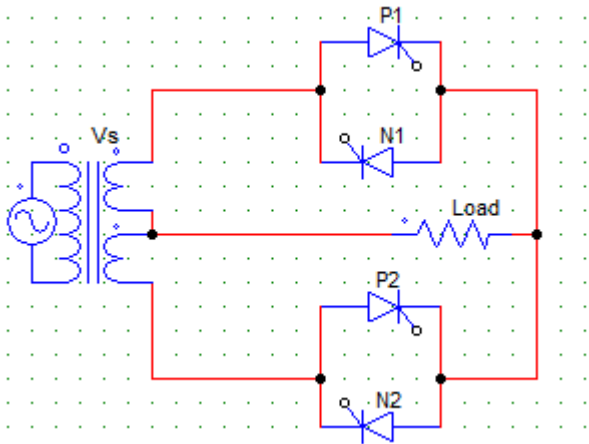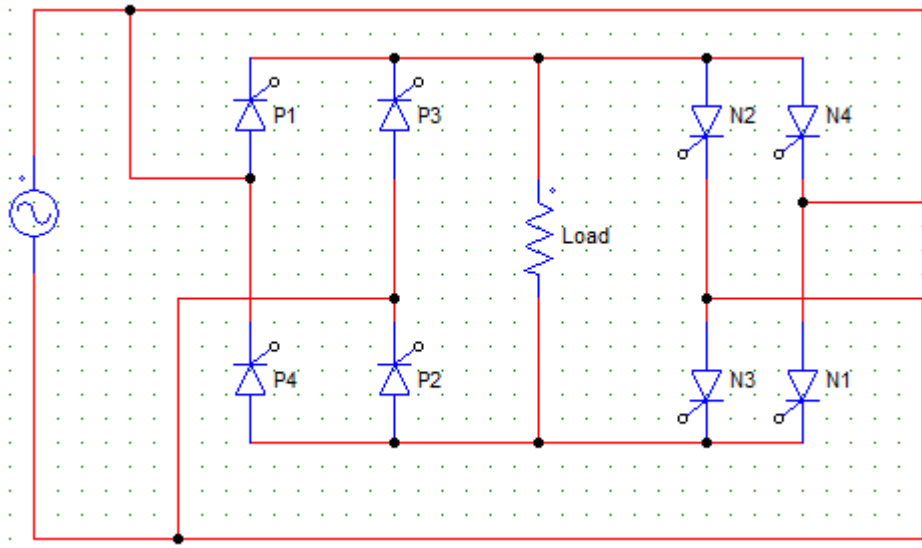	c) P1 and N2 are forward biased d) None of the mentioned
6	In the below given cycloconverter circuit, _____ and _____ conduct in one cycle together.  a) P1, P2 and N1, N2 b) P1, N2 and N1, P2 c) N1, P1 and N1, P2 d) None of the mentioned
7	In the positive half cycle, _____ SCRs are forward biased.  a) P1, P2, N1, N2 b) P1, P2, P3, P4 c) N1, N2, N3, N4 d) P3, P4, N1, N2
8	The principle of three phase cycloconverter is to a) add and remove number of SCRs b) vary progressively the firing angle of the devices c) keep the firing angle as 0° for all the devices d) none of the mentioned
9	In three phase cycloconverters, the reduction factor is given by a) input frequency/output frequency b) (input frequency/output frequency)⁻¹

	c) (input frequency/output frequency) $^{-1/2}$ d) (input frequency/output frequency) $^{1/2}$
10	In a three phase half-wave cycloconverter _____ a) both inverting and converting action takes place b) only inversion action takes place c) only converting action takes place d) none of the mentioned
11	A cycloconverter is a (a) Frequency changer from higher to lower frequency with one-state conversion (b) Frequency changer from higher to lower frequency with two-stage conversion (c) Frequency changer from lower to higher frequency with one-stage conversion (d) Either a or c
12	The cycloconverter require natural or forced commutation as under (a) Natural commutation in both step-up and step down cycloconverter (b) Forced commutation in both step-up and step-down cycloconverter (c) Forced commutation in step-up cycloconverter (d) Forced commutation in step-down cycloconverter
13	The quality of output ac voltage of a cycloconverter is improved with a) Increase in output voltage at reduced frequency b) Increase in output voltage at increased frequency c) decrease in output voltage at reduced frequency d) decrease in output voltage at increased frequency
14	four quadrant chopper cannot be operated as a) One quadrant chopper b) Cycloconverter c) Inverter d) Bidirectional rectifier
15	A cycloconverter converts: a) AC to DC b) DC to AC c) DC to DC with different level d) AC to AC at different frequencies
16	AC voltage controllers convert a) fixed ac to fixed dc b) variable ac to variable dc c) fixed ac to variable ac d) variable ac to fixed ac
17	In AC voltage controllers the a) variable ac with fixed frequency is obtained b) variable ac with variable frequency is obtained c) variable dc with fixed frequency is obtained d) variable dc with variable frequency is obtained
18	Earlier then the semiconductor technology, _____ devices were used for voltage control applications. a) cycloconverters b) vacuum tubes c) tap changing transformer d) induction machine

19	The AC voltage controllers are used in _____ applications. a) power generation b) electric heating c) conveyor belt motion d) power transmission
20	In the principle of phase control a) the load is on for some cycles and off for some cycles b) control is achieved by adjusting the firing angle of the devices c) control is achieved by adjusting the number of on off cycles d) control cannot be achieved
21	A single-phase half wave voltage controller consists of a) one SCR is parallel with one diode b) one SCR is anti parallel with one diode c) two SCRs in parallel d) two SCRs in anti parallel
22	Pulse gating is suitable for a) R loads only b) R and RL loads c) RL loads only d) all types of loads
23	In continues gating a) overlap angle is very high b) SCR is heated up c) size of the pulse transformer is small d) commutation cannot be achieved effectively
24	High frequency gating uses a a) train of pulses b) continuous gating block c) carrier signal d) none of the above
25	A single-phase sinusoidal voltage controller has a) one primary and n secondary windings b) one primary and (n-1) secondary windings c) n primary and n secondary windings d) (n-1) primary and n secondary windings
26	Sequence control of ac voltage controllers is employed for the improvement of _____ a) output frequency b) input frequency c) commutation d) system power factor
27	A two stage sequence control is a) two SCRs in anti parallel b) two voltage controllers in parallel c) two voltage controllers in series d) a voltage controller having two voltage level
28	From the below given statements regarding sequence control of ac voltage, which of them are true? i) It improves system power factor ii) It reduces the harmonic content at the output

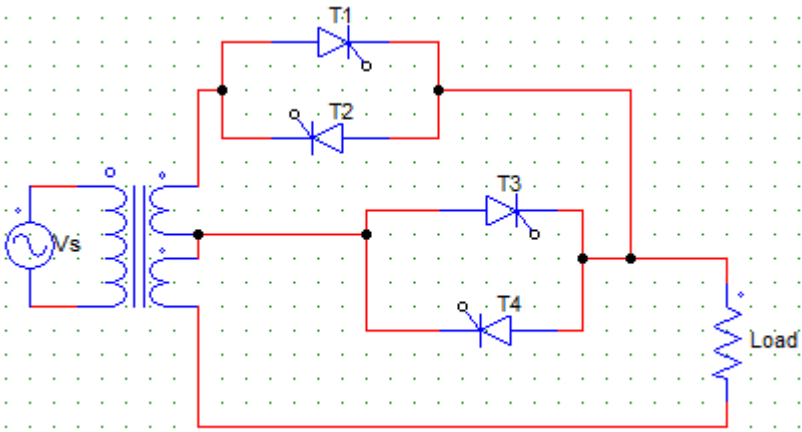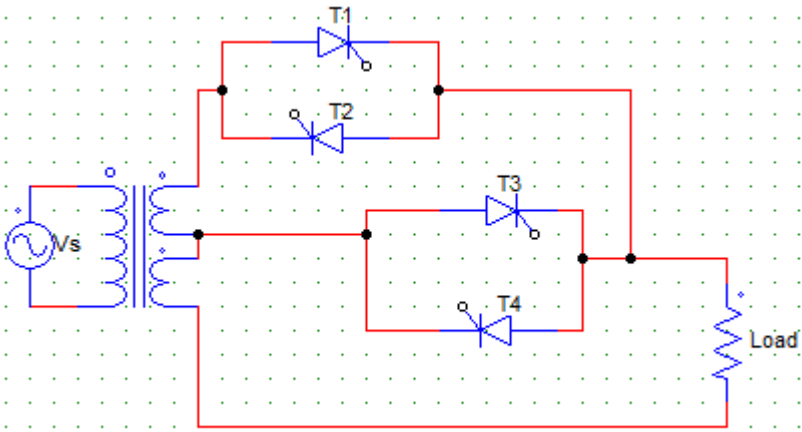	iii) Wider control of output voltage is possible a) only (i) b) only (i) and (ii) c) only (i) and (iii) d) all of them are true
29	The below given circuit is that of a  a) four stage sequence controller b) two stage sequence controller c) full wave ac voltage controller d) none of the mentioned
30	If T1, T2 are kept off and T3, T4 are having a firing angle of 180° each, then the output voltage is _____ if the turns ratio is 1:1  a) V_s b) $\sqrt{2}V_s$ c) 0 d) $2V_s$

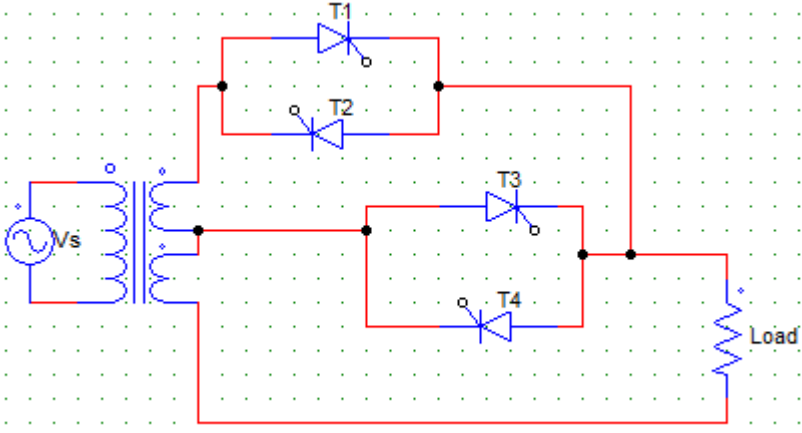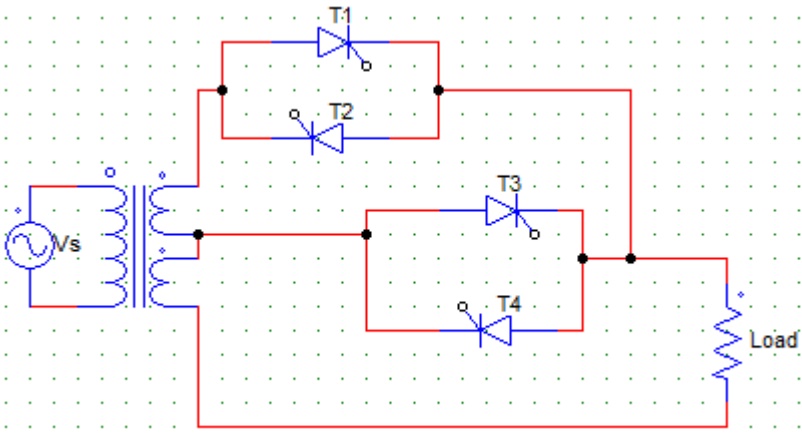31	For obtaining the output voltage control from V to $2V$, the firing angle must be  a) always 0 for T3, T4 b) always 180 for T3, T4 c) 0 to 180 from T3, T4 d) none of the mentioned
32	For obtaining the output voltage control from V to $2V$, the firing angle must be  a) always 0 for T1, T2 b) always 180 for T1, T2 c) 0 to 180 from T1, T2 d) none of the mentioned
33	In a N-stage sequence controller, each secondary is rated for _____ a) $n \times V_s$ b) V_s c) V_s/n d) $V_s \times (n-1)$
34	The converter circuit which employs turn on and turn off when the voltage and/or current through the device is zero at the instant of switching is _____ a) a conventional converter b) a resonant converter c) a zero switching circuit d) none of the mentioned
35	TRIAC is used in a) chopper b) speed control of induction machine

	c) speed control of universal motor d) none of the mentioned
--	--